

8. (a) Write the elementary calculations of energy consumption in electricity supply system. 8
- (b) Write a short note on Battery Back-up. 7
9. (a) What is the difference between loop and mesh in an electrical circuit ? 2
- (b) What is power factor and its importance ? 3
- (c) Why is ammeter always connected in series ? 2
- (d) Write the concept of Slip in Three Phase Induction Motor. 3
- (e) Discuss the different types of Batteries. 3
- (f) What is the difference between wire and a cable ? 2

No. of Printed Pages : 04

Roll No.

18A11

B. Tech. EXAMINATION, 2022

(Second Semester)

(C Scheme) (Main & Re-appear)

EE101C

BASIC ELECTRICAL ENGINEERING

(Common for All Branches)

Time : 3 Hours]


[Maximum Marks : 75

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.

Note : Attempt *Five* questions in all, selecting *one* question from each Unit. Q. No. **9** is compulsory.

Unit I

1. (a) State and drive the Kirchhoff's current and voltage law equations with circuit diagram. 7
- (b) State the Norton's theorem with circuit diagram. 8
2. Find the current in each branch using nodal analysis in the circuit given below : 15

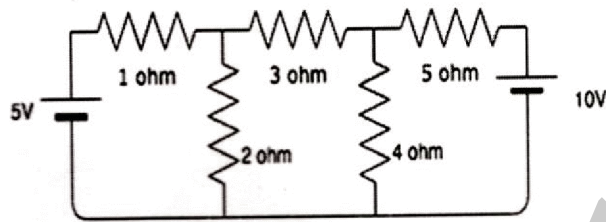

Unit II

3. Two elements in series circuit are connected across $V = 5 \sin (314t + 120^\circ)$ V and current equation is $I = 15 \sin (314t + 150^\circ)$ A. Find out Resistance, Inductance, Impedance, Power Factor, Active Power, Reactive Power. 15

4. (a) Write the relation between Line Voltage and Phase Voltage for Star connections. 7
- (b) Explain the time domain analysis of first order RC series circuit. 8

Unit III

5. Explain the construction and working of single phase transformer. Draw the phasor diagram of ideal transformer for resistive, inductive and capacitive load. 15
6. (a) Explain the construction and working principle of synchronous generator. 8
- (b) Write the construction and working of capacitor start single phase induction motor. 7

Unit IV

7. Write short notes on the following :
 - (a) Earthing and its importance 7
 - (b) MCB and MCCB. 4+4