

5. (a) Explain the behaviour of shunt RLC circuit for AC signal. 7.5

(b) Differentiate between balanced and unbalanced 3-phase AC circuits. 7.5

Unit III

6. (a) Draw the phasor diagram for a real transformer with capacitive load. 7.5

(b) Derive EMF equation of a transformer. 7.5

7. Describe construction, working principle and types of three-phase induction motors with suitable diagrams. 15

Unit IV

8. (a) Explain different types of wires and cables which are used for connections in Electrical and Electronics appliances. 7.5

No. of Printed Pages : 05

Roll No.

18A11

B.Tech. EXAMINATION, 2022

(First Semester)

(C Scheme) (Main & Re-appear)

(Common for all Branches)

EE101C

BASIC ELECTRICAL ENGINEERING

Time : 3 Hours]

[Maximum Marks : 75

Before answering the question-paper candidates should ensure that they have been supplied to correct and complete question-paper. No complaint, in this regard, will be entertained after the examination.


Note : Q. No. 1 is compulsory. Attempt *Four* more questions from the remaining questions, selecting *one* question from each Unit.

1. (a) What is the difference among resistance, reactance and impedance ? **2.5**
- (b) Define Q-factor. **2.5**
- (c) What is the difference between active and reactive powers ? **2.5**
- (d) What is use of slip ring ? **2.5**
- (e) What is difference between phase and line currents ? **2.5**
- (f) Why power of a electric source is represented in VA instead of Watt ? **2.5**


Unit I

2. (a) Derive formulate for star to delta and delta to star conversion. **7.5**
- (b) Explain superposition theorem. Explain its practical application also. **7.5**

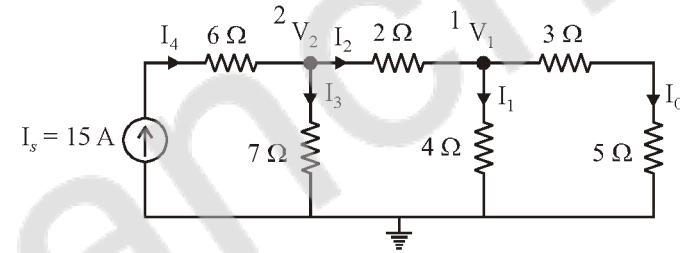3. (a) In the following circuit, find out the current across $4\ \Omega$ resistance using nodal analysis. **7.5**



- (b) In the following circuit, using Norton's theorem, find out current across R_L . **7.5**

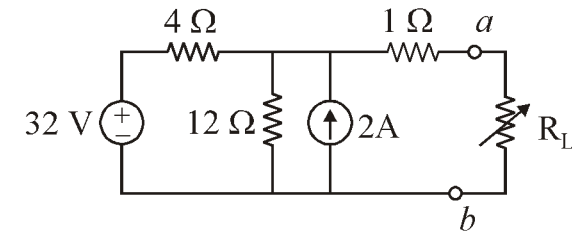

Unit II

4. (a) Calculate average value of a half wave rectified signal. **7.5**
- (b) Derive Q-factor of series resonant circuit. **7.5**

- (b) Explain different types of batteries. Also explain their specific applications. **7.5**

9. Write notes on the following :

- (a) ELCB **7.5**
(b) MCCB. **7.5**

- (b) Explain different types of batteries. Also explain their specific applications. **7.5**

9. Write notes on the following :

- (a) ELCB **7.5**
(b) MCCB. **7.5**